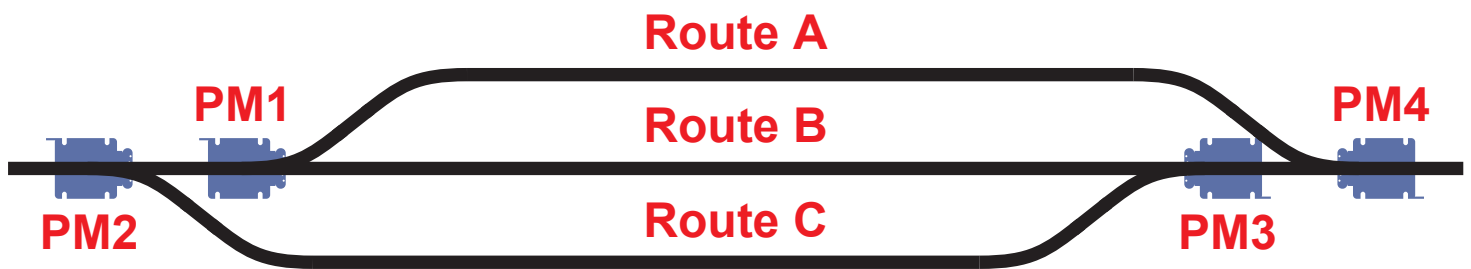


# LAYOUT

## CONCEPTS

### Route Setting With Push Button Switches Controlling A Diode Matrix & iP Digital Point Motors







Cobalt iP Digital Point Motor - DCP-CBDiP

PM2

PM1

PM3

PM4

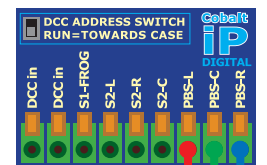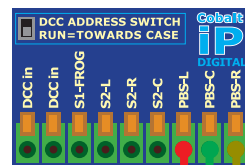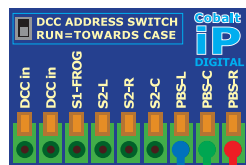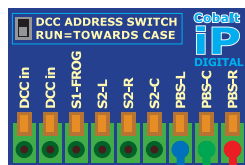

Route A

Route B

Route C

Alpha Push Button Switch DCD-APB

The diodes are 1N4001 or similar